

EveryCircuit Assignment: Basic MOSFET Circuits

In this assignment you will analyze a collection of basic MOSFET circuits. For each circuit, you will do the following:

1. Use MOSFET equations to predict the DC operating point.
2. For amplifier circuits, calculate small-signal parameters g_m , r_o , and predict the amplifier gain.
3. Simulate using EveryCircuit and compare the results to your calculations.
4. Take a screenshot showing the EveryCircuit simulation.

Throughout this assignment you will use the default MOSFET parameters from EveryCircuit:

	NMOS	PMOS
K	590u	454.5u
Vth	0.43	0.4
lambda	0.06	0.1

Additionally, you will use these circuit parameters for each problem:

- $V_{DD} = 10V$
- $I_B = 100\mu A$

Problem 1: NMOS Current Mirror

For the NMOS current mirror shown below, the desired bias current is I_B , and the current delivered to the load is I_L . Determine the required bias resistor R , calculate the gate voltage V_G , and predict the drain voltage and current on the load side, V_D and I_L respectively.

Enter your calculations in the table below. Then simulate the circuit and enter measured values in the table. If the simulations are very different from the calculations, you should check your work for mistakes.

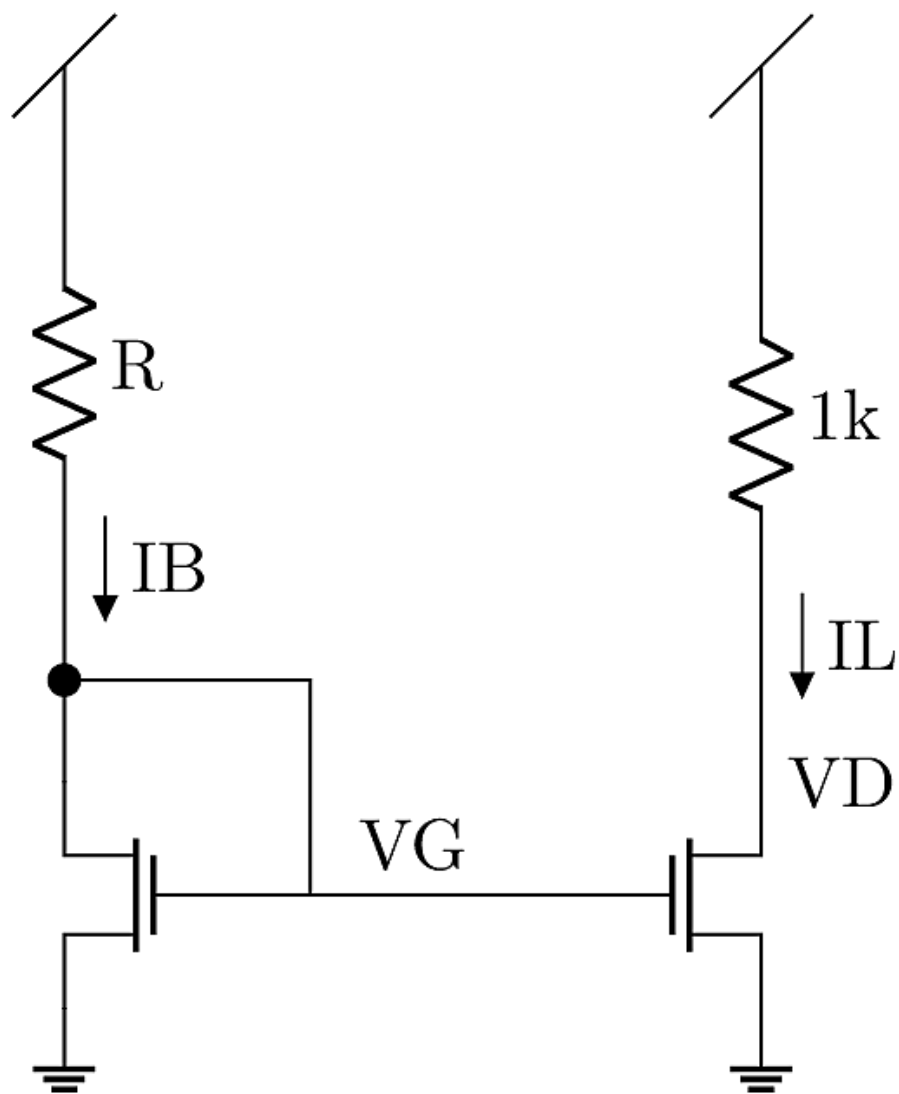


Figure 1: NMOS current mirror circuit.

Calculation	Simulation
R	
VG	
IL	
VD	

Attach a screenshot of the EveryCircuit simulation showing your measurements.

Problem 2: NMOS Passive-Bias Amplifier

Now modify the NMOS current mirror circuit to create the amplifier shown below. Note that the 1k load resistor is now replaced with a duplicate of your bias resistor R. The signal source should have a zero-to-peak amplitude of 5mV and a frequency of 1kHz. Calculate the small-signal parameters g_m , r_o , and the amplifier's gain, then compare to simulation results.

Enter your calculations in the table below. Then simulate the circuit and enter measured values in the table. If the simulations are very different from the calculations, you should check your work for mistakes.

Calculation	Simulation
g_{mn}	X
r_{on}	X
A_v	

Attach a screenshot of the EveryCircuit simulation showing your measurements.

Problem 2: NMOS Ideal Active-Bias Amplifier

Now modify the NMOS current mirror circuit to create the amplifier shown below. Note that the load resistor is now replaced with an ideal current source. The signal source should have a zero-to-peak amplitude of 5mV and a frequency of 1kHz. Calculate the small-signal parameters g_m , r_o , and the amplifier's gain, then compare to simulation results.

Enter your calculations in the table below. Then simulate the circuit and enter measured values in the table. If the simulations are very different from the calculations, you should check your work for mistakes.

Calculation	Simulation
g_{mn}	X
r_{on}	X

Calculation	Simulation
A_v	

Attach a screenshot of the EveryCircuit simulation showing your measurements.

Problem 4: PMOS Current Mirror

For the PMOS current mirror shown below, the desired bias current is I_B , and the current delivered to the load is I_L . Determine the required bias resistor R , calculate the gate voltage V_G , and predict the drain voltage and current on the load side, V_D and I_L respectively.

Enter your calculations in the table below. Then simulate the circuit and enter measured values in the table. If the simulations are very different from the calculations, you should check your work for mistakes.

Calculation	Simulation
R	
V_G	
I_L	
V_D	

Attach a screenshot of the EveryCircuit simulation showing your measurements.

Problem 5: PMOS Passive-Bias Amplifier

Now modify the PMOS current mirror circuit to create the amplifier shown below. Note that the $1k$ load resistor is now replaced with a duplicate of your bias resistor R . The signal source should have a zero-to-peak amplitude of $5mV$ and a frequency of $1kHz$. Calculate the small-signal parameters g_m , r_o , and the amplifier's gain, then compare to simulation results.

Enter your calculations in the table below. Then simulate the circuit and enter measured values in the table. If the simulations are very different from the calculations, you should check your work for mistakes.

Calculation	Simulation
g_m	X
r_o	X
A_v	

Attach a screenshot of the EveryCircuit simulation showing your measurements.


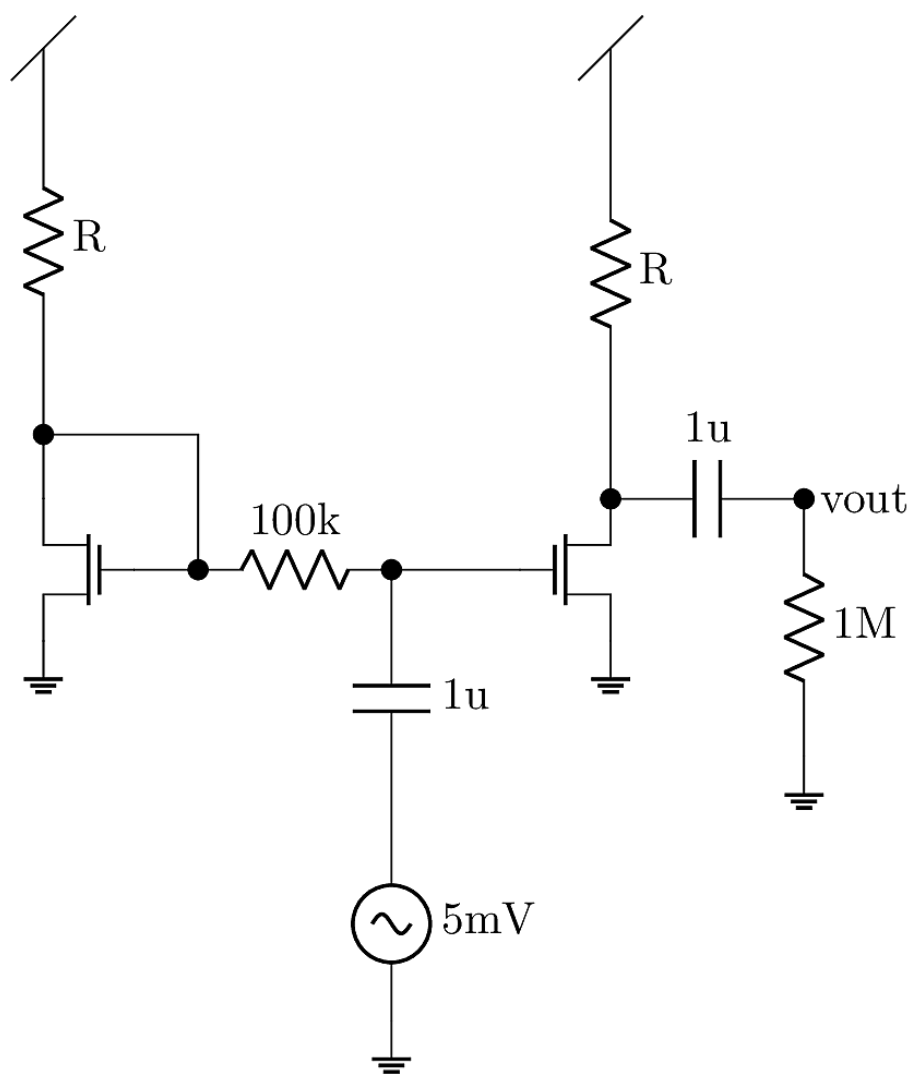


Figure 2: NMOS passive-bias amplifier circuit.

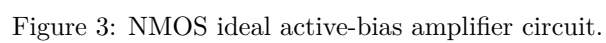

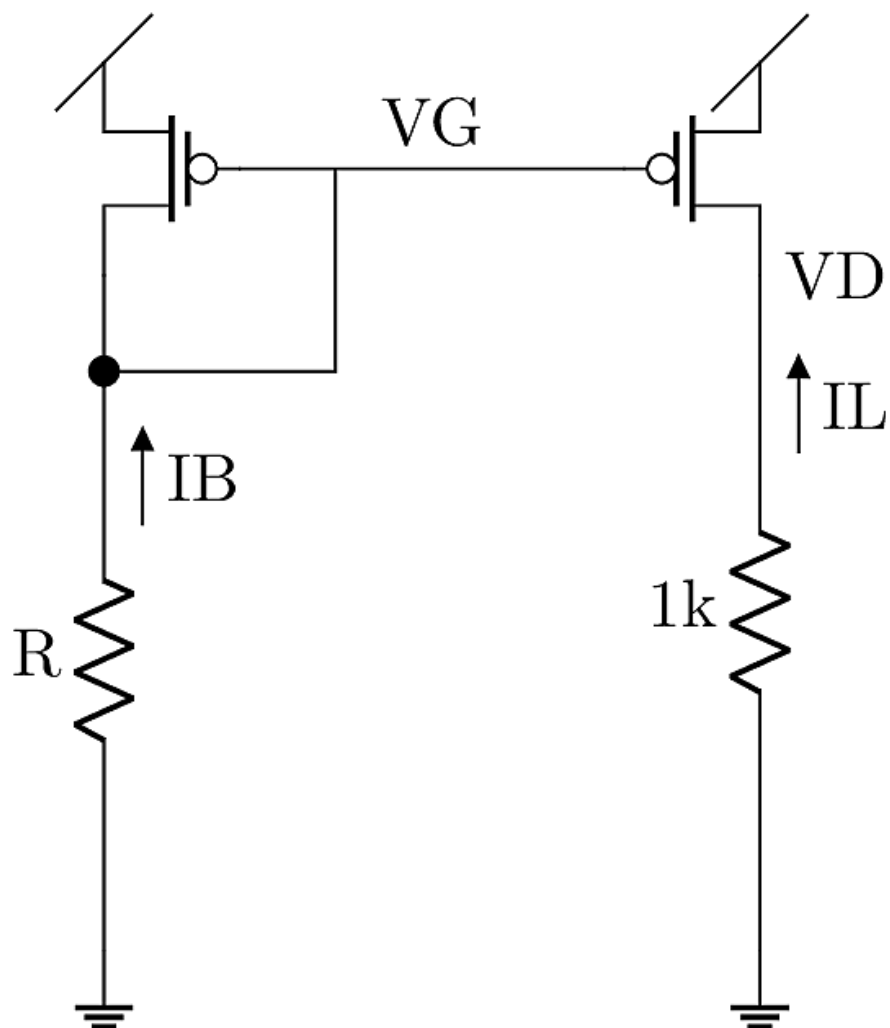


Figure 4: PMOS current mirror circuit.

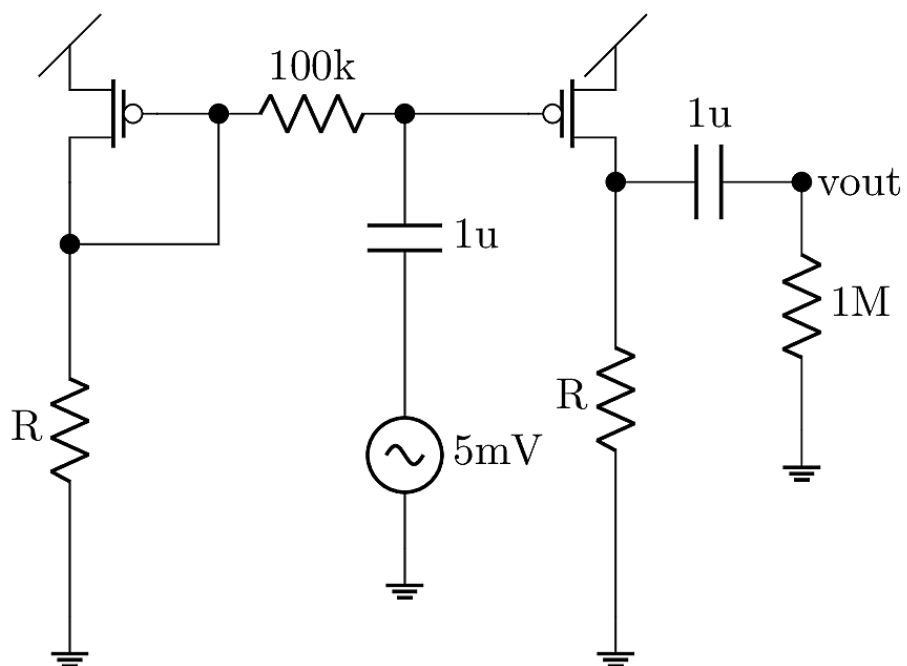


Figure 5: PMOS passive-bias amplifier circuit.

Problem 6: PMOS Ideal Active-Bias Amplifier

Now modify the PMOS current mirror circuit to create the amplifier shown below. Note that the load resistor is now replaced with an ideal current source. The signal source should have a zero-to-peak amplitude of 5mV and a frequency of 1kHz. Calculate the small-signal parameters g_m , r_o , and the amplifier's gain, then compare to simulation results.

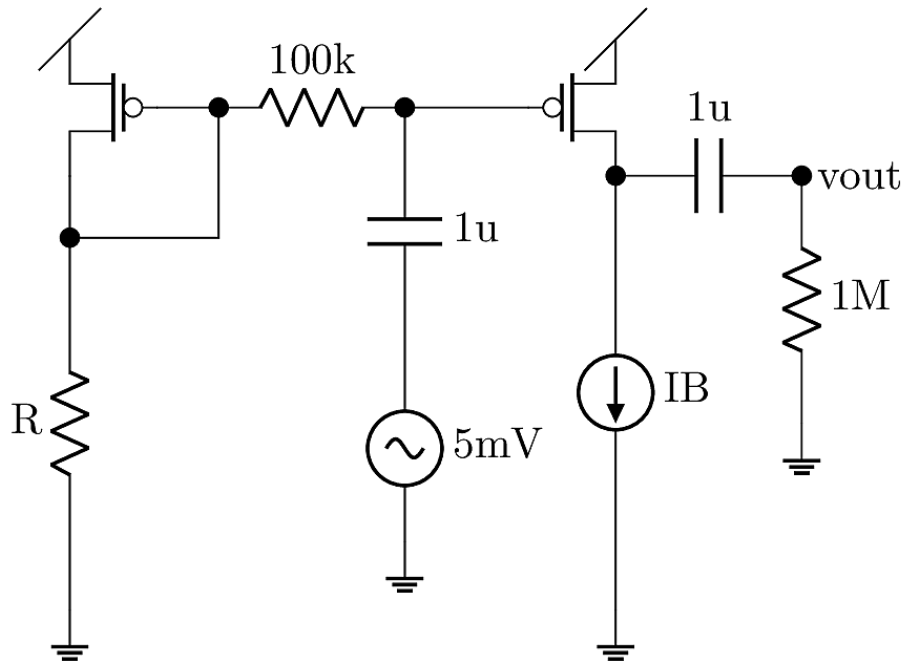


Figure 6: PMOS ideal active-bias amplifier circuit.

Enter your calculations in the table below. Then simulate the circuit and enter measured values in the table. If the simulations are very different from the calculations, you should check your work for mistakes.

	Calculation	Simulation
g_{mp}		X
r_{op}		X
A_v		

Attach a screenshot of the EveryCircuit simulation showing your measurements.

Problem 7: CMOS Active-Bias Amplifier

Now you will combine NMOS and PMOS mirrors to create a practical amplifier circuit. This circuit is called a “Complementary” MOS or “CMOS” amplifier because it combines both device polarities. For this circuit, you can re-use calculations for R , g_m and r_o . Using those calculations, predict the amplifier’s gain and confirm the result using EveryCircuit.

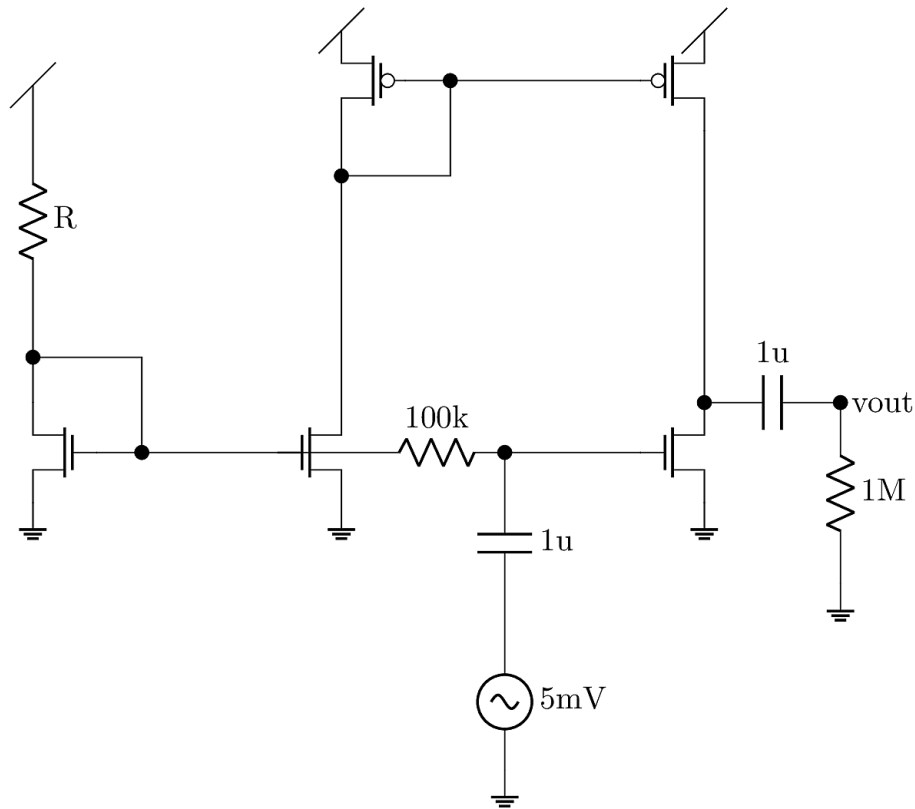


Figure 7: CMOS active-bias amplifier circuit.

Calculation	Simulation
A_v	

Attach a screenshot of the EveryCircuit simulation showing your measurements.