

Calvin Passmore

A02107892

ECE 5420


DRAM Lab Report

PMOS Width

Here is my calulations

$$W_p = W_n \left(\frac{u_n}{u_p} \right) \left(\frac{V_{thn} - V_{dd}/2}{V_{thp} - V_{dd}/2} \right)^2$$
$$W_p = (1u)(524/202.5) \left(\frac{0.7086 - 3.3/2}{0.918 - 3.3/2} \right)^2$$
$$W_p = 3.4 \text{ } \mu\text{m}$$

The simulation gave the following:

 

Resulting in a PMOS width of approximately 3.4 μm

Inverter Crossover Voltage

Doing the calculations, $V_c = 1.69 \text{ v}$

$$V_c = (\sqrt{K_n} + V_{thn} + \sqrt{K_p} * (V_{dd} - |V_{thp}|)) / (\sqrt{K_n} + \sqrt{K_p})$$

```
from math import sqrt
```

```
KN = 261e-6
```

```
KP = 331e-6
```

```
VTHN = 0.7086
```

```
VTHP = 0.918
```

```
VDD = 3.3
```

```
Vc = ((sqrt(KN) * VTHP) + (sqrt(KP) * (VDD - VTHP))) / (sqrt(KN) + sqrt(KP))
```


```
print(Vc)
```

$V_c = 1.6934$

Doing the simulation gives us

DC Response

Thu Dec 8 13:26:40 2022 1

 

$V_c \approx 1.69$ v

Tail Current and Reference Resistor

```
x = Vdd/2 = 1.65
```

```
Vgsp = Vdd/2 = 1.65
```

```
Vovp = Vdd/2 = Vthp = 1.65 - 0.918 = 0.73 -> saturation
```

```
id = 0.5 * Kp * Vov^2 = 88.7 uA
NMOS -> 88.7 = 0.5 * Kn * Vovn^2 => Vovn = sqrt(2*88.7 u / 261u) = 0.481 v
Vgs - Vthn = 0.481 => Vgs = 0.481 + Vthn = 1.189 => Vg - Vs = 1.65 - Vs
Vs = 1.65 - 1.19 = 0.461 v
```

NMOS at the bottom of the OTA

```
id = 2 * 88.7 uA = 177.4 uA
177.4 = 0.5 * Kn * Vov^2 => Vov = 0.961
Vgs - Vth = Vg - Vs - Vthn where Vs = GND
Vg = 0.961 + Vthn = 1.669
```


NMOS in series with the resistor

```
id = 0.5 * Kn * Vov^2 = 0.5 * Kn * (Vgs - Vthn) = 120.5 uA
R = (3.3 - 1.669) / 120.5 uA = 13.5 kOhm
```

The Virtuoso Simulation gives


DC Response

Thu Dec 8 13:33:22 2022 1

 

13.5 kOhm

Complete the crossbar address decoder

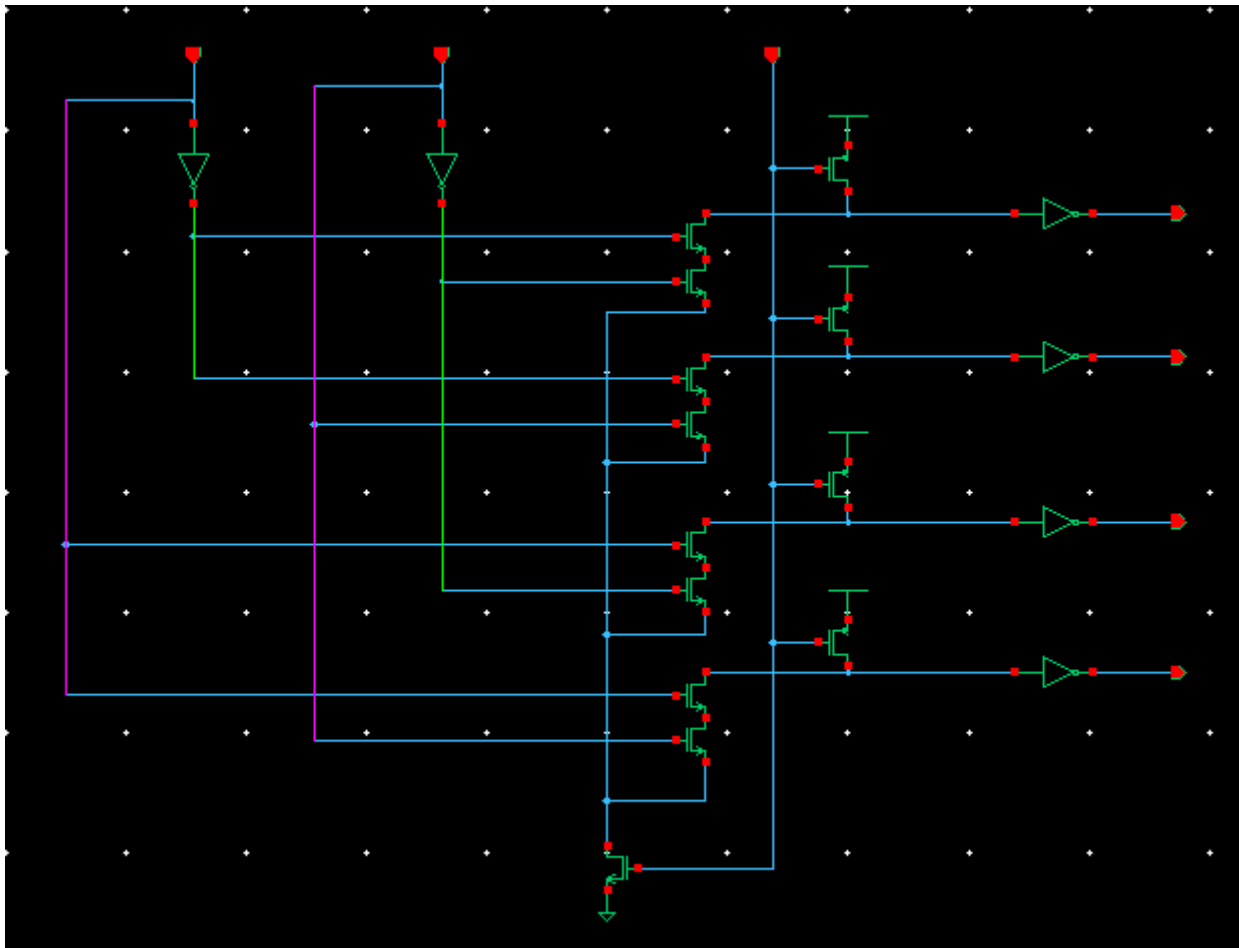

Predict the Bump Voltage


```
CD = 30e-15
CBL = 3e-12
VDD = 3.3
VTH = 0.7086

V1 = (((VDD/2) - VTH) * CD) / (CBL + CD)
V0 = (-CD * VDD / 2) / (CBL + CD)

print(f"Vbump 1 = {V1}")
print(f"Vbump 0 = {V0}")
```



V1 = 9.3mV V0 = -16mV



The simulation gives this


 



V1sim ≈ 20mV V0sim ≈ 40mV

  Below are the measurements for WL, BL, S and D



  

  

 

Changing the capacitance to 131p breaks the DRAM where it reads a wrong value. 130p also showed significant signal loss, but still well above $V_{dd}/2$

